# De Morgan's Laws

Author:Shefali Garg 11678 CSE

November 5, 2012

#### Table of contents

**Logic Gates** 

And Gate

Or Gate

Not Gate

De Morgan's laws

Prove De Morgan's Laws

First Law

Second Law

Generalised De Morgan's laws

References

### **And Gate**

For any two given inputs A and B,output X is given as X=AB

Figure : AND gate

Truth table for AND gate [2]

Α	В	Χ
1	1	1
1	0	0
0	1	0
0	0	0

### Or Gate

For any two given inputs A and B,output X is given as X=A+B

Figure: Or gate

$$A \xrightarrow{\qquad \qquad } X$$

Truth table for Or gate [4]

Α	В	Χ	
1	1	1	
1	0	1	
0	1	1	
0	0	0	

### **Not Gate**

For given input A,output X is given as  $X = \overline{A}$ 

Figure: Not gate



## Truth table for not gate [1]

Α	Х
1	0
0	1

# De morgan's laws for two variables

Let A and B be two inputs. Then by De Morgan's laws [3],

$$\overline{A+B} = \overline{A} \overline{B}$$

$$\overline{AB} = \overline{A} + \overline{B}$$

### Prove of First Law

According to first law,an OR gate with all inputs inverted (a Negative-OR gate) behaves the same as a NAND gate that is,  $\overline{AB} = \overline{A} + \overline{B}$ 

Figure: First Law

$$\begin{array}{c|c} A & AB \\ \hline B & is equivalent to \\ \hline A & \overline{A} \\ \hline B & \overline{B} & \overline{A} + \overline{B} \end{array}$$

#### This can be proved by truth table

Α	В	ĀB	Ā	$\overline{B}$	$\overline{A} + \overline{B}$
1	1	0	0	0	0
1	0	1	0	1	1
0	1	1	1	0	1
0	0	1	1	1	1

### Proof of Second Law

According to first law,an AND gate with all inputs inverted (a Negative-AND gate) behaves the same as a NOR gate that is,  $\overline{A+B}=\overline{A}~\overline{B}$ 

Figure: Second Law

$$\begin{array}{c} A+B \\ B \\ \hline \\ Is equivalent to \\ A \\ \hline \\ B \\ \hline \\ \end{array} \begin{array}{c} \bar{A}+\bar{B} \\ \bar{A}\bar{B} \\ B \\ \hline \end{array}$$

#### This can be proved by truth table

Α	В	$\overline{A+B}$	Ā	B	$\overline{A}\overline{B}$
1	1	0	0	0	0
1	0	0	0	1	0
0	1	0	1	0	0
0	0	1	1	1	1



# De morgan's laws for n variables

Let  $x_1, x_2, ..., x_n$  be two inputs. Then,

$$\overline{X_1 + X_2 + ... + X_n} = \overline{X_1 X_2} ... \overline{X_n}$$

#### References

- John Bird.

  Engineering Mathemetics.

  Newness, Reading, Stanford, 1999.
- Jaegar.

  Microelectronic Circuit Design.

  McGraw-Hill, Reading, Massachusetts, 1997.
- De Morgan.
  The Comprehensive Tex Archive Network (CTAN).

  TUGBoat, 14(3):342–351, 1999.
- Richard F Tinder.

  Engineering digital design: Revised Second Edition.

  McGraw-Hill, Reading, Massachusetts, 1990.